

[By OnlineInterviewQuestions.com](http://OnlineInterviewQuestions.com)

Take Analog Electronics Quiz To test your Knowledge

Below are few **Analog Electronics MCQ** test that checks your basic knowledge of Asp.Net. This **Analog Electronics Test** contains around 20 questions of multiple choice with 4 options. You have to select the right answer to a question. apart from this, you can also download Analog Electronics MCQ PDF completely free.

Q1. Whenever load is coupled class A amplifier through transformer efficiency

- A. Increases
- **B. Decreases**
- C. Nothing happen

Q2. When MOSFET switch is its on-state it is equivalent to

- A. resistor
- **B. capacitor**
- C. inductor
- D. battery

Q3. The units of transistor h parameters h11 and h22 are

- **A. Same**
- B. Different

Q4. A buffer amplifier should have

- A. low input impedance and high output impedance
- **B. high input impedance and high output impedance**
- C. high input impedance and low output impedance
- D. low input impedance and low output impedance

Q5. When the ac base voltage in a CE amplifier circuit is too high, the ac emitter current is

- A. constant
- **B. distorted**
- C. alternating
- D. zero

Q6. A voltage with square waveform having values of +5V and 0V is

- A. wifi signal
- **B. digital signal**
- C. current signal
- D. analog signal

Q7. As the ratio R_f/R_L increases the efficiency of a rectifier increases.

- **A. True**
- B. False

Q8. In a transistor CE mode, $V_{CC} = +30\text{ V}$. If the transistor is in cut off region, $V_{CE} =$

- **A. +30 V**
- B. +20 V
- C. 10 V
- D. 0 V

Q9. In all base driver amplifiers

- **A. ac emitter voltage is 180° out of phase with ac base voltage**
- B. ac collector voltage is in phase with ac base voltage
- C. ac collector voltage is 180° out of phase with ac base voltage
- D. none of the above

Q10. A 10 V power supply would use which filter capacitor?

- A. paper capacitor
- **B. electrolytic capacitor**
- C. mica capacitor
- D. air capacitor

Q11. What is the condition if no external potential energy is applied to the PN junction then diode ?

- A. Forward biased
- B. Reversed biased
- **C. Zero Bias**
- D. None of These

Q12. What is an energy gap?

- **A. Space between two orbital shells**
- B. Energy band in which electrons can move freely
- C. Energy level at which an electron can exist
- D. None of the above

Q13. What will happen if doping of an intrinsic semiconductor with pentavalent impurity atom ?

- A. Fermi level not change
- B. Fermi level fall
- **C. Fermi level raises**
- D. All of the above

Q14. Silicon has _____ valence electrons.

- A. 2
- **B. 4**
- C. 6
- D. 8

Q15. _____ does not obey the Ohm's law.

- A. Resistor
- B. Bilateral device
- **C. Semiconductor**
- D. None of the above

Q16. When the JFET is no longer able to control the current, this point is called the -

- A. depletion region.
- B. pinch-off region
- C. saturated point.
- **D. breakdown region**

Q17. When the drain saturation electric current is less than I_{DSS} a JFET acts like a -

- **A. current source**
- B. BJT
- C. battery
- D. resistor

Q18. In the active region, the collector current is not changed significantly by -

- A. base current
- B. base supply voltage
- **C. collector resistance.**
- D. current gain

Q19. The current gain of a transistor is defined as the ratio of the collector current to the -

- A. emitter current
- **B. base current**
- C. supply current
- D. collector current

Q20. Three different Q points are shown on a load line. The upper Q point represents the -

- **A. maximum current gain**
- B. minimum current gain
- C. intermediate current gain
- D. cutoff point

Please Visit OnlineInterviewquestions.com to download more pdfs