

# By OnlineInterviewQuestions.com

## Circuit Theorems In Ac Analysis MCQ Test

### Take Circuit Theorems In Ac Analysis MCQ Test & Online Quiz to test your Knowledge

Below is the **Circuit Theorems In Ac Analysis MCQ** test that checks your basic knowledge of Circuit Theorems In Ac Analysis. This **Circuit Theorems In Ac Analysis MCQ Test** contains 20 Multiple Choice Questions. You have to select the right answer to the question. Finally, you can also take the Online Quiz from the Take **Circuit Theorems In Ac Analysis Quiz** Button.

**Q1. Which of the following are the two basic components of a Thevenin equivalent ac circuit?**

- A. the equivalent voltage source and the equivalent series resistance
- B. the equivalent voltage source and the equivalent parallel resistance
- **C. the equivalent voltage source and the equivalent series impedance**
- D. the equivalent voltage source and the equivalent parallel resistance

**Q2. What is the Norton equivalent current?**

- **A. The short circuit current**
- B. The current through the load
- C. The open-current from the source
- D. None of the above

**Q3. The superposition theorem is useful for circuit analysis only in ac circuits.**

- A. True
- **B. False**

**Q4. The superposition theorem is useful for the analysis of single-source circuits.**

- A. True
- **B. False**

**Q5. The Norton equivalent current is \_\_\_\_.**

- A. The current through the load
- B. The open-circuit current from the source
- **C. The short circuit current**
- D. None of the above

**Q6. The Thevenin equivalent voltage is:**

- A. Equal to the source voltage
- B. The same as the load voltage
- **C. The open circuit voltage**
- D. None of the above

**Q7. A Thevenin ac equivalent circuit always consists of an equivalent ac voltage source and an equivalent capacitance.**

- **A. True**
- B. False

**Q8. In order to get maximum power transfer from a capacitive source, the load must have a/an \_\_\_\_.**

- A. capacitive reactance equal to circuit resistance
- **B. impedance that is the complex conjugate of the source impedance**
- C. capacitive as it is inductive
- D. None of the above

**Q9. Like Thevenin's theorem, Norton's theorem provides a method of reducing a more complex circuit to a simpler, more manageable form for analysis.**

- **A. True**
- B. False

**Q10. Norton's theorem gives:**

- A. an equivalent voltage source in series with an equivalent impedance
- **B. an equivalent current source in parallel with an equivalent impedance**
- C. an equivalent current source in series with an equivalent impedance
- D. an equivalent voltage source in parallel with an equivalent impedance

**Q11. \_\_\_ and \_\_\_ theorems provide methods for reducing a circuit to a simple equivalent form for easier analysis.**

- **A. Thevenin's, Norton's**
- B. Newton's and Norton's theorems
- C. Thevenin's and Ohm's theorems
- D. None of the above

**Q12. An equivalent circuit is one that produces the same voltage and current to a given load as the original circuit that it replaces.**

- **A. True**
- B. False

**Q13. Is AC Analysis is used to calculate the small-signal response of a circuit?**

- **A. Yes**
- B. No

**Q14. In applying the superposition theorem, \_\_\_.**

- **A. the sources are considered one at a time with all others replaced by their internal impedance**
- B. all sources are considered simultaneously
- C. the sources are considered one at a time with all others replaced by their internal resistance
- D. all sources are considered independently

**Q15. Which one of the following is not the step to analyze an AC circuit?**

- A. Transform the circuit to the phasor or frequency domain.

- B. Solve the problem using method analysis or theorem circuit techniques.
- C. Transform the resulting phasor to the time domain.
- D. None of the above

**Q16. In an ac circuit, power to the load peaks at the frequency at which the load impedance is the complex conjugate of the output impedance.**

- A. True
- B. False

**Q17. Is Thevenin's theorem, as applied to ac circuits, provides a method for reducing any circuit to an equivalent form that consists of an equivalent ac voltage source in series with an equivalent impedance?**

- A. Yes
- B. No

**Q18. Thevenin's equivalent voltage is defined as the \_\_\_\_\_ between two specified terminals in a circuit.**

- A. open circuit voltage
- B. closed circuit voltage
- C. open circuit current
- D. None of the above

**Q19. What do you mean by Norton's equivalent current?**

- A. the open-circuit current between two specified terminals in a given circuit.
- B. the short-circuit current between two specified terminals in a given circuit
- C. total current between two specified terminals in a given circuit.
- D. None of the above

**Q20. The complex conjugate of  $50 \angle 0^\circ + j100 \angle 0^\circ$  is**

- A.  $50\angle -j50 \text{ } \Omega$ ;
- B.  $100\angle +j50 \text{ } \Omega$ ;
- C.  $100 \angle -j50$
- **D.  $50 \angle -j100 \text{ } \Omega$ ;**

Please Visit [OnlineInterviewquestions.com](http://OnlineInterviewquestions.com) to download more pdfs