

# By OnlineInterviewQuestions.com

## Digital Electronics MCQ Quiz

### Take Digital Electronics Quiz To test your Knowledge

Practice below the best **Digital Electronics MCQ Questions** that checks your basic knowledge of Digital Electronics. This **Digital Electronics MCQ Test** contains 20+ Multiple Choice Questions. You have to select the right answer to every question to check your final preparation for your exams. Apart from this, you can also download the **Digital Electronics MCQ PDF** completely free.

**Q1. which of the following is Universal Gate?**

- A. OR gate
- **B. NAND gate**
- C. AND gate
- D. NOR gate

**Q2. Which of the following is Inverter?**

- A. OR gate
- **B. NOT gate**
- C. AND gate
- D. NAND GATE

**Q3. The NOR gate is OR gate followed by which gate ?**

- A. AND gate
- **B. NOT gate**
- C. NAND gate
- D. None of the mentioned

**Q4. In the boolean algebra, a variable has \_\_\_\_\_ different state(s)/value(s).**

- A. 3
- B. 1
- **C. 2**

- D. 4

**Q5. AND operation is equivalent to -**

- **A. Intersection**
- B. Division
- C. Union
- D. none of the above

**Q6.  $A + ?$  is  $= ?$**

- A. 0
- **B. 1**
- C. A
- D. ?

**Q7. Which is the example of digital device from the given option ?**

- A. Record players
- **B. Microprocessors**
- C. Sensors
- D. Thermistors

**Q8. \_\_\_\_\_ numbers are used in the decimal number system?**

- **A. 0 to 9**
- B. 0 to 10
- C. 1 to 10
- D. None of the above

**Q9. Combinations that not listed for the input variables are -**

- A. Borrow
- **B. Don't Care**
- C. Overflow
- D. Carry

**Q10. A full adder have -**

- A. 2 inputs, 2 outputs
- B. 2 inputs, 1 output
- **C. 3 inputs, 2 outputs**
- D. 3 inputs, 1 output

**Q11. In Positive logic, logic gate 1 corresponds to -**

- A. Zero Voltage Level
- B. Positive Voltage
- C. Lower Voltage Level
- **D. Higher Voltage Level**

**Q12. An X-OR Gate Produces an output only when it's two inputs are -**

- A. Low
- **B. Different**
- C. Same
- D. High

**Q13. The Only Function of a Not gate is to -**

- **A. Invert an input signal**
- B. Stop A signal
- C. Act an universal set
- D. Re complement a signal

**Q14. ASCII code is a ..... bit code.**

- A. 8
- **B. 7**
- C. 2
- D. 1

**Q15. Multiplexer means .....**

- **A. Many in to One**
- B. Many in to Many
- C. One in to Many
- D. None of the Above

**Q16. Binary Number system has ..... symbols.**

- A. 8
- B. 16
- C. 10
- **D. 2**

**Q17. The Steps required for the analysis of combinational circuits are -**

- A. Obtain the functions of intermediate points and outputs
- B. Label the inputs and outputs
- C. Draw the truth table
- **D. All of the Above**

**Q18. There are two types of parity -**

- A. Odd
- B. Even
- **C. Both 1 & 2**
- D. None of the above

**Q19. The Four common and useful MSI circuits are**

- A. Decoder
- B. Encoder
- C. Demultiplexer
- **D. All of the above**

**Q20. .... Multiplexers can be constructed from smaller ones.**

- **A. Larger**
- B. Small
- C. Dimultiplexers

- **D.** None of the above

Please Visit [OnlineInterviewquestions.com](http://OnlineInterviewquestions.com) to download more pdfs